```
-- Company:
-- Engineer:
-- Create Date: 02/01/2024 02:05:09 PM
-- Design Name:
-- Module Name: compunit - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
-- Dependencies:
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.std logic unsigned.ALL;
USE IEEE.numeric std.ALL;
--use IEEE.std logic unsigned.all;
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

```
entity compunit is
Port (a,b:in std logic vector(5 downto 0);
 s: in std logic vector(4 downto 0);
 o:out std logic vector(5 downto 0));
end compunit;
architecture Behavioral of compunit is
begin
process (A,B,s)
begin
case s is
when"00000"=>0 < = A and B;
when"00001"=>o<=A or B;
when"00010"=>o<=A nand B;
when"00011"=>o<=A nor B;
when"00100"=>o<=A xor B;
when"00101"=>o<=A xnor B;
when"00110"=>o<=A + B;
when"00111"=>o<=A - B;
when"01000"=>o<=
std logic vector(to unsigned(to integer(unsigned(a)) *
to integer (unsigned(b)), 6));
when "01001" \Rightarrow if (A > B) then o <= "1111111"; else o <= "000000"; end
if;
when "01010" \Rightarrow if (A < B) then o <= "1111111"; else o <= "000000"; end
if;
when "01011" \Rightarrow if (A = B) then o <= "1111111"; else o <= "000000"; end
if;
when "01100" \Rightarrow if (A \Rightarrow B) then o \Leftarrow "111111"; else o \Leftarrow "000000"; end
if;
when "01101" \Rightarrow if (A <= B) then o <= "1111111"; else o <= "000000"; end
if;
when"01110"=> if(A /= B) then o <= "1111111"; else o <= "000000";end
```

```
if;
when"01111"=> o <="000000";
when "10000" => o <= to_stdlogicvector(to_bitvector (a) sla
TO INTEGER (unsigned (b));
when "10001" => o <= to stdlogicvector(to bitvector (a) sra
TO INTEGER (unsigned (b));
when "10010" => o <= to stdlogicvector(to bitvector (a) srl
TO INTEGER (unsigned (b));
when "10011" => o <= to stdlogicvector(to bitvector (a) sll
TO INTEGER (unsigned (b)));
when "10100" => o <= to stdlogicvector(to bitvector (a) ror
TO INTEGER (unsigned (b));
when "10101" => o <= to stdlogicvector(to bitvector (a) rol
TO INTEGER (unsigned (b));
when others => o <= (others => '0');
end case;
end process;
end Behavioral;
```